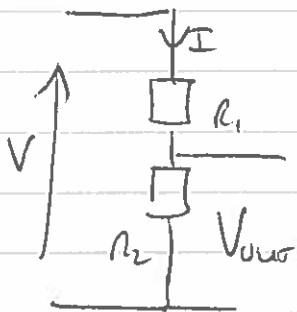


## Intro Questions


a) Ohm's Law  $V = IR$   
 $\Rightarrow V = I(R_1 + R_2)$



$$V_{out} = I R_2$$

$$\Rightarrow \frac{V_{out}}{V} = \frac{R_2}{R_1 + R_2} \quad V_{out} = \frac{R_2}{R_1 + R_2} V$$

(POTENTIAL DIVIDER)

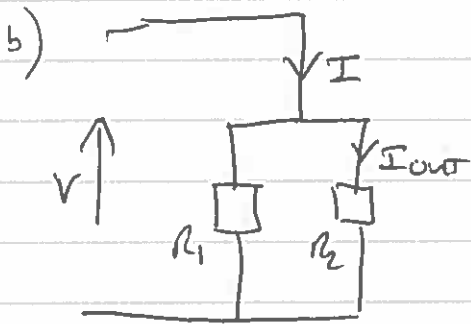

$$I_{out} = \frac{V}{R_2}$$

$$I = \frac{V}{R_1 // R_2}$$

IN PARALLEL


$$R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$= \frac{V(R_1 + R_2)}{R_1 R_2}$$

$$\Rightarrow \frac{I_{out}}{I} = \frac{R_1}{R_1 + R_2}$$

$$I_{out} = \frac{R_1}{R_1 + R_2} I$$

CURRENT DIVIDER

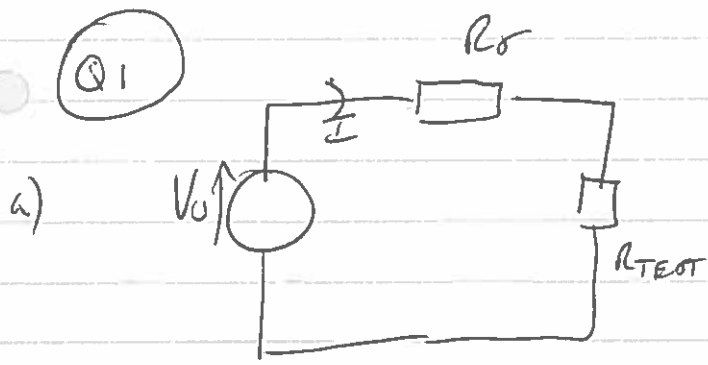

	$V_{\text{out}}$	$I$
$R_{\text{TEST}1}$	600V	0.4A
$R_{\text{TEST}2}$	650V	0.2A

$\Rightarrow$  Voltage round loop sum = 0

$$\Rightarrow V_0 - 0.4 R_s = 600 \quad (\text{TEST 1})$$

$$V_0 - 0.2 R_s = 650 \quad (\text{TEST 2})$$

$$\Rightarrow V_0 = 700 \text{ V} \quad R_s = 250 \Omega$$



	$I_{\text{out}}$	$V_{\text{out}}$
$R_{\text{TEST}1}$	0.4A	600V
$R_{\text{TEST}2}$	0.2A	650V

$\Rightarrow$  Sum currents into node at top

$$\Rightarrow I_0 = I_{\text{out}} + \frac{V_{\text{out}}}{R_s}$$

$$I_0 = 0.4 + 600/R_s$$

$$I_0 = 2.8 \text{ A}$$

$$R_s = 250 \Omega$$


$$I_0 = 0.2 + 650/R_s$$

$R_s$  is the same as in part (a). Use Norton transformation to get

$$V_0 = I_0 R_s$$

Q2


Battery #1

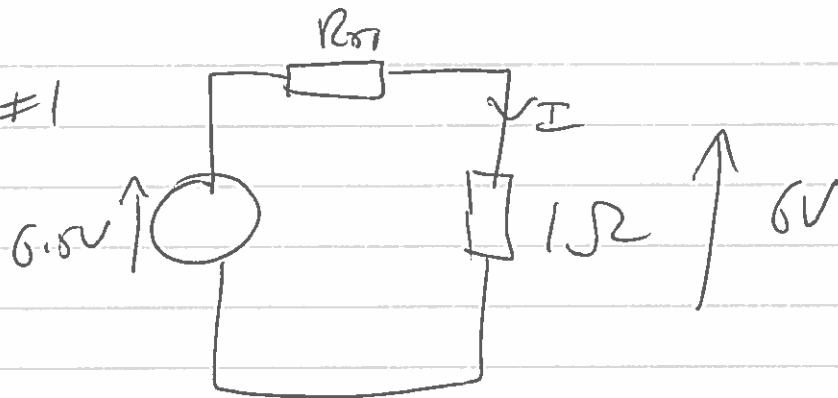

$$\Rightarrow I = \frac{6V}{1\Omega} = 6A \quad 0.5V \text{ drop across } R_{01}$$
$$R_{01} = \frac{6.5 - 6.0}{6} = 0.0833\Omega$$

Similarly for other Batteries  $R_{02} = 0.0656\Omega$   
 $R_{03} = 0.0909\Omega$

b) For Battery #1 take Norton equivalent

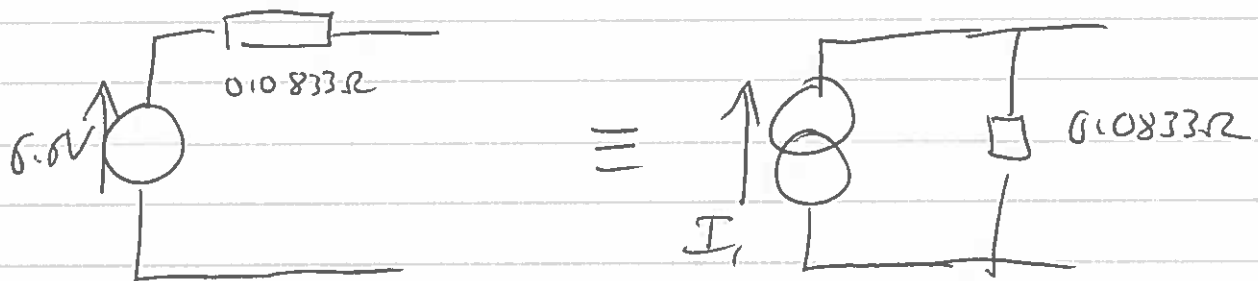


$$I_1 = \frac{6.5}{0.0833} = 78A \quad \left( \text{note/ this current is not real, it's the current that would flow if the battery were shorted} \right)$$

Similarly for other Batteries

$$I_2 = \frac{6.5V}{0.0656\Omega} = 99.12A \quad I_3 = \frac{6V}{0.0909\Omega} = 66A$$

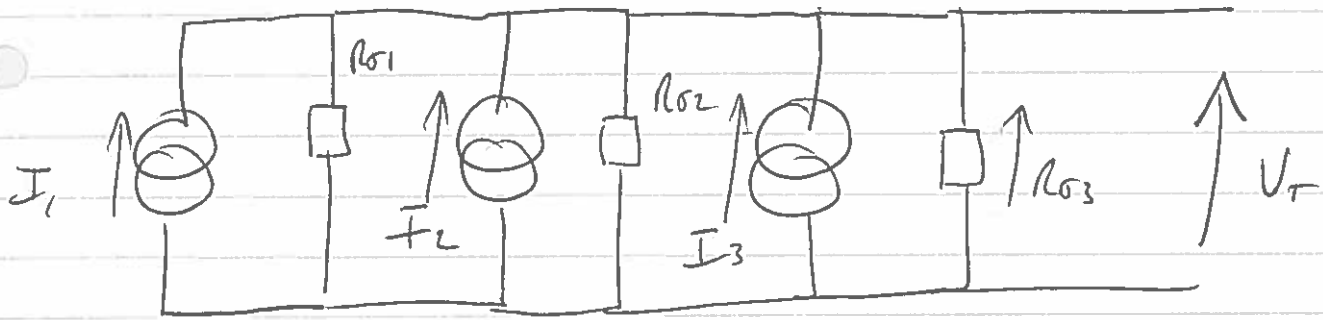All three batteries can ~~the~~ now be connected in parallel to find the combined current and resistance.




$$I_T = \sum I = I_1 + I_2 + I_3 = 243.1 \text{ A}$$


$$R_T = R_{01} \parallel R_{02} \parallel R_{03} = \left[ \frac{1}{R_{01}} + \frac{1}{R_{02}} + \frac{1}{R_{03}} \right]^{-1}$$

$$= 0.0261 \Omega$$

Total combined cct

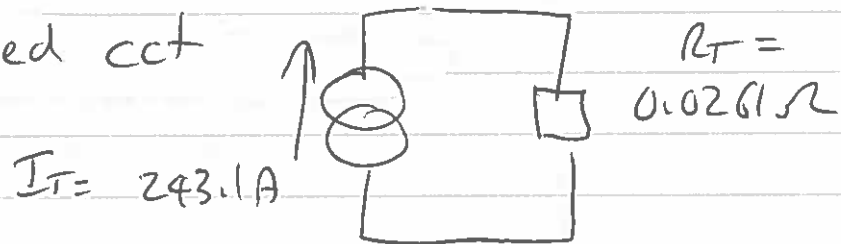


Thévenin

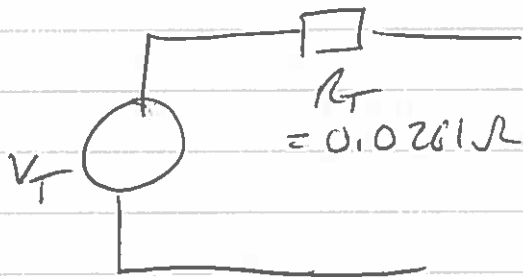

$$V_T = I_T R_T$$

$$= 6.36 \text{ V}$$

Original Circuit

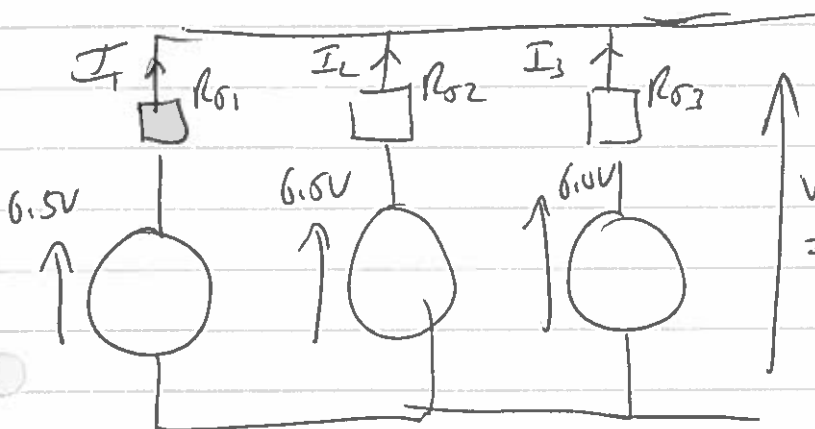

$$I_1 = \frac{6.5 - 6.36}{R_{01}} = 1.73 \text{ A}$$


$$I_2 = \frac{6.5 - 6.36}{R_{02}} = 2.19 \text{ A}$$

$$I_3 = \frac{6.0 - 6.36}{R_{03}} = -3.92 \text{ A}$$

↑  
note -ve  
(opposite direction)


$$\sum I = I_1 + I_2 + I_3 = 0 \text{ As expected.}$$

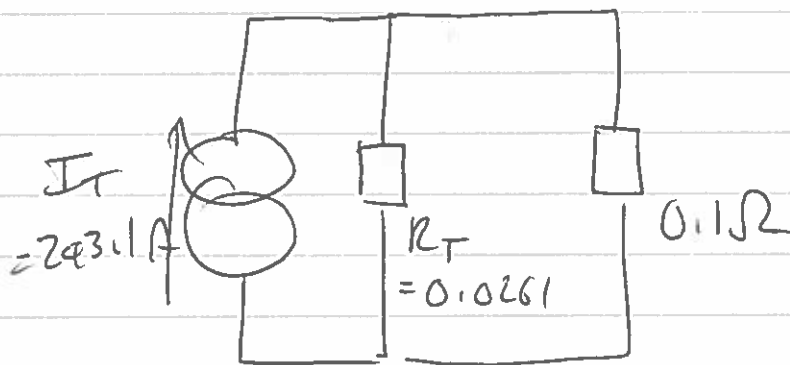- c) Simplest approach is to return to the Norton equivalent of the 3 batteries.



↑ new voltage with load connected =  $V'$

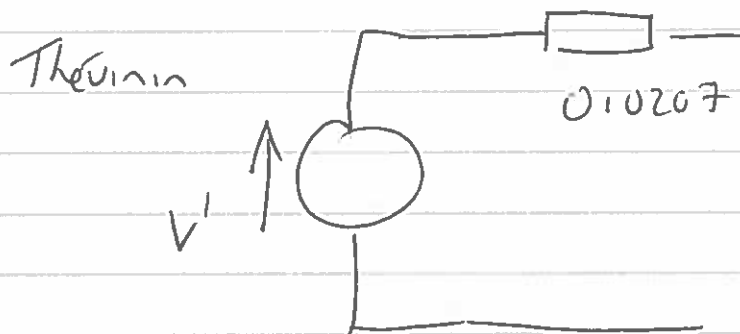⇒ Total resistance =  $R_T // 0.1 \Omega = 0.0207 \Omega$



$$V' = 243.1 \times 0.0207 = 5.04 \text{ V}$$

New currents from batteries are now:

$$I_1 = \frac{6.5 - 5.04}{R_{S1}} = 17.5 \text{ A}$$

$$I_2 = \frac{6.5 - 5.04}{R_{S2}} = 22.3 \text{ A}$$

$$I_3 = \frac{6.0 - 5.04}{R_{S3}} = 10.6 \text{ A}$$

check

$$\Sigma I \text{ at node} \Rightarrow I_1 + I_2 + I_3 = 50.4 \text{ A} = \frac{V'}{0.1} = \frac{5.04}{0.1} \quad \checkmark$$

nb/ The accuracy of answer will depend on how many decimal places are used in calculations.

d) Voltage across  $0.1 \Omega$  load =  $V' = 5.04 \text{ V}$

$$\Rightarrow \text{Power} = \frac{V^2}{R} = \frac{5.04^2}{0.1} = 254 \text{ W}$$

For each battery the power dissipated =  $I^2 R$

Battery 1  $P_1 = I_1^2 R_{s1} = 25.15 \text{ W}$


$$P_2 = I_2^2 R_{s2} = 32.6 \text{ W}$$

$$P_3 = I_3^2 R_{s3} = 10.2 \text{ W}$$

Total power on batteries =  $68.3 \text{ W}$

Compared to power into the load this is not very efficient  
(21 %)

Q3 a) Nodal analysis

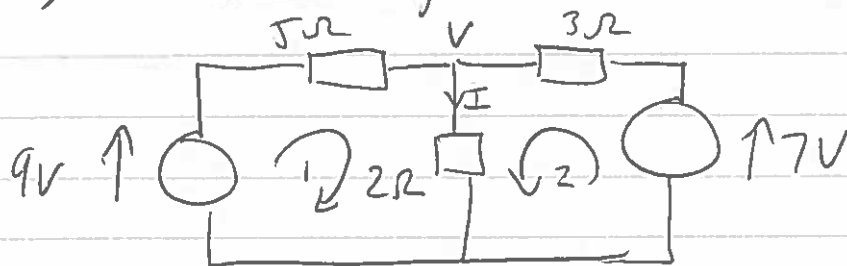

$$\frac{9-V}{5} + \frac{7-V}{3} + \frac{0-V}{2} = 0$$

$$\Rightarrow 54 - 6V + 70 - 10V - 15V = 0 \quad V = 4\text{V} \quad I = 2\text{A}$$

b) Mesh analysis loop ①  $9 - 5I_1 - 2(I_1 + I_2) = 0$   
 $9 - 7I_1 - 2I_2 = 0$

$$\text{Loop 2} \quad 7 - 3I_2 - 2(I_1 + I_2) = 0$$

$$7 - 2I_1 - 5I_2 = 0$$

Solve simultaneous eqn (use calc!)

$$\Rightarrow I_1 = 1 \text{ A} \quad I_2 = 1 \text{ A}$$

$$I = I_1 + I_2 = 2 \text{ A}$$

$$V = 4 \text{ V}$$

④ Easiest way is to assume all current are going into each node and are positive. Sum currents to zero (Kirchhoff).

$$\text{Node (A)} \quad +4 \text{ A} + \frac{0 - V_A}{4} + \frac{V_C - V_A}{2} + \frac{V_B - V_A}{1/2} = 0$$

$$\times 4 \quad 16 - 11V_A + 8V_B + 2V_C = 0 \quad (i)$$

$$\text{Node (B)} \quad \frac{V_A - V_B}{1/2} + \frac{0 - V_B}{3} + \frac{V_C - V_B}{1} = 0$$

$$\times 3 \quad 6V_A - 10V_B + 3V_C = 0 \quad (ii)$$

$$\text{Node (C)} \quad +2 \text{ A} + \frac{V_B - V_C}{1} + \frac{0 - V_C}{1/2} + \frac{V_A - V_C}{2} = 0$$

$$\times 2 \quad 4 + V_A + 2V_B - 7V_C = 0 \quad (iii)$$


Note, we want current through the top  $2\Omega$  resistor hence we need  $V_A$  &  $V_C$ , not  $V_B$ , Eliminate  $V_B$  first.

use calculator  $\therefore$  (ii) +  $5 \times$  (iii)  
 (i) -  $4 \times$  (iii)

To get  $V_A = 4V$   $V_C = 2V$

$\Rightarrow$  Current in  $2\Omega = 1A$

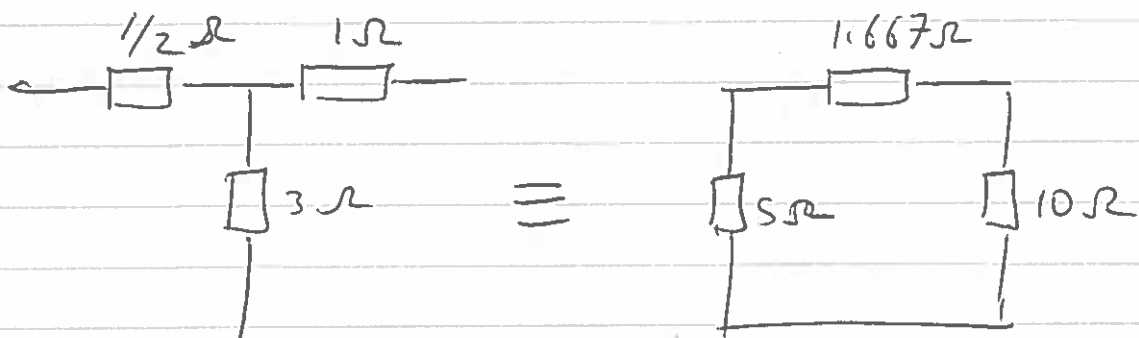
Q5 Star  $\rightarrow$  Delta transformation (in data book)




Star

Delta

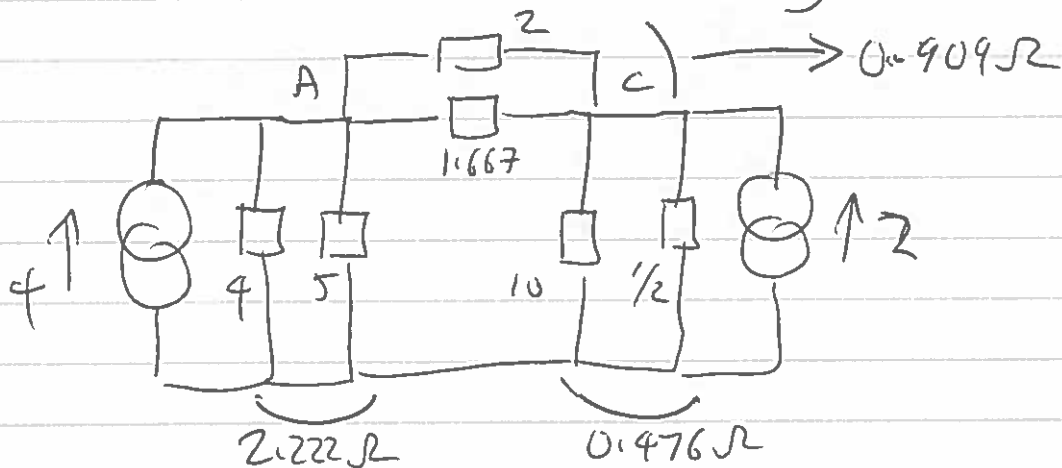Replace Central 3 resistors in Fig 4 with delta



Thévenin

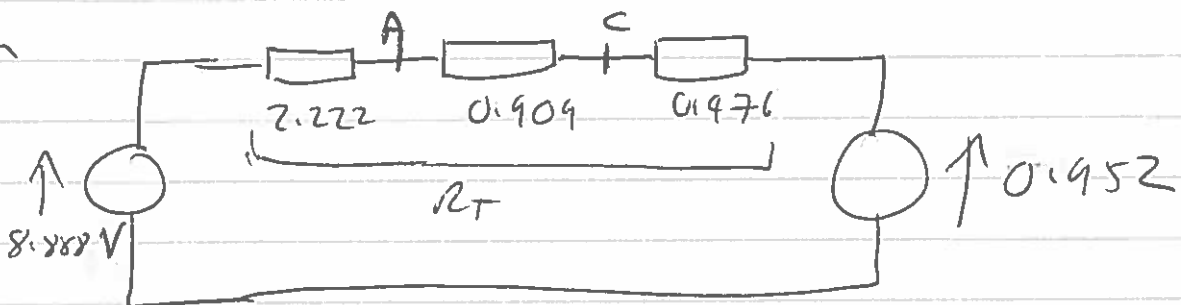



Converted cct has only 2 nodes (earth)

$$\Rightarrow 1 + \frac{0 - V_x^2}{0.5} + \frac{V_p - V_x^1}{1} = 0 \quad 1 + V_p - 3V_x = 0 \quad (i)$$


note sign as it is coming out of the node.

$$-20 + \frac{0 - V_p^3}{1/3} + \frac{V_x - V_p^1}{1} = 0 \quad -20 - 4V_p + V_x = 0 \quad (ii)$$

$$(i) + 3 \times (ii) \quad -59 - 11V_p = 0$$

$$V_p = -59/11 \text{ V} \\ (-5.36 \text{ V})$$

Q7

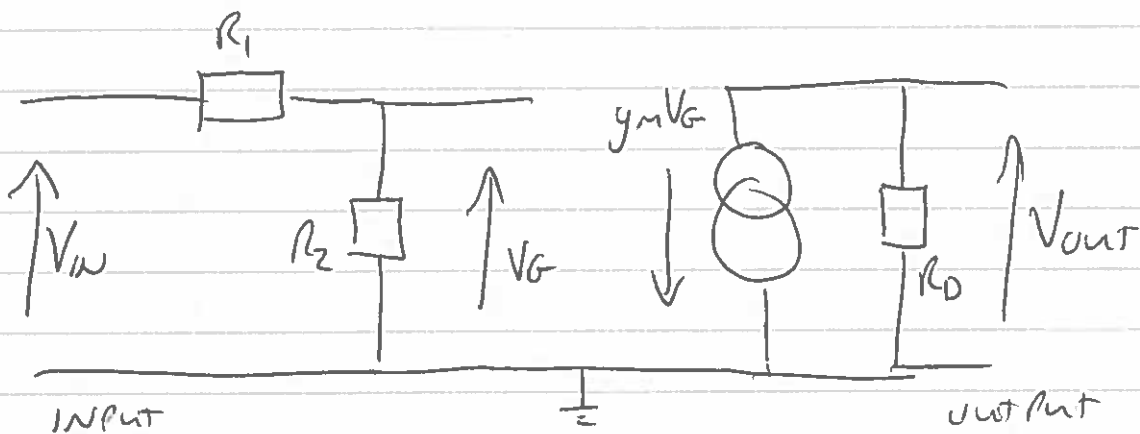

At input we have a potential divider such that

$$V_G = \frac{R_2}{R_1 + R_2} V_{IN}$$

At the output current  $g_m V_G$  must go through  $R_D$  but note the direction of the current with respect to the direction of  $V_{out}$

$$g_m V_G = \frac{0 - V_{out}}{R_D} \Rightarrow V_{out} = -g_m V_G R_D$$


$$\text{Total } R = R_T = 3.607 \Omega$$

$$\text{Current through } R_T = \frac{8.888 - 0.452}{3.607} = 2.20 \text{ A}$$

$$\text{Voltage between node A \& C} = 2.20 \times 0.909 = 2 \text{ V}$$

$$\Rightarrow \text{current through } 2 \Omega = 1 \text{ A} \quad \checkmark$$

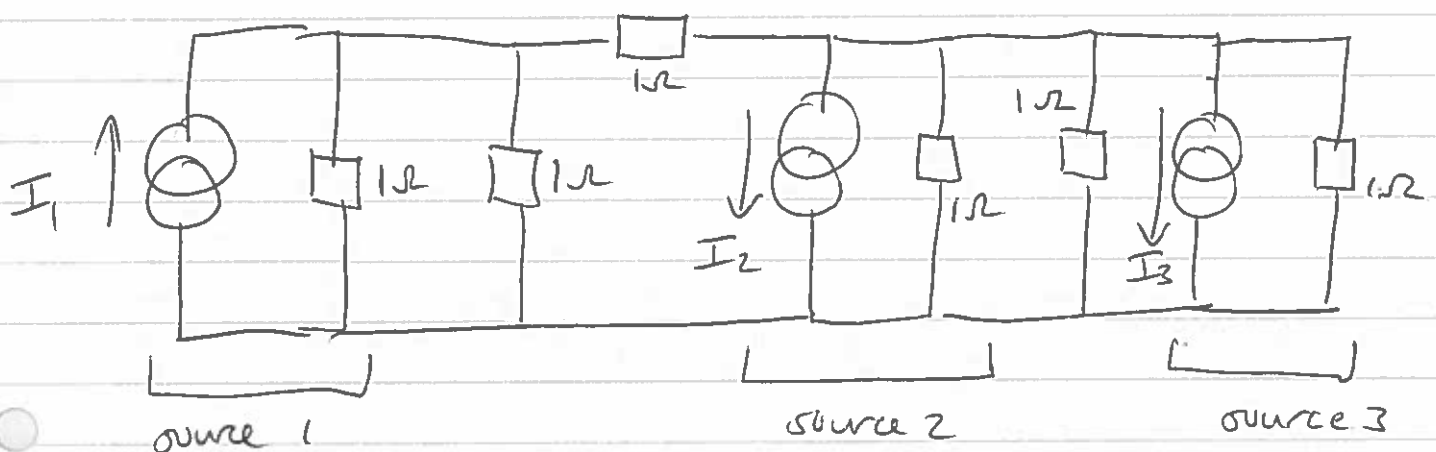
Q6 4 loops would be required  $\Rightarrow$  4 sets of equations to solve. If we apply Norton equivalent to sources then it becomes:



$$I_1 = 1 \text{ A} \quad I_2 = 10 \text{ A} \quad I_3 = 10 \text{ A}$$

note direction of  $I_2$  &  $I_3$  (-ve)

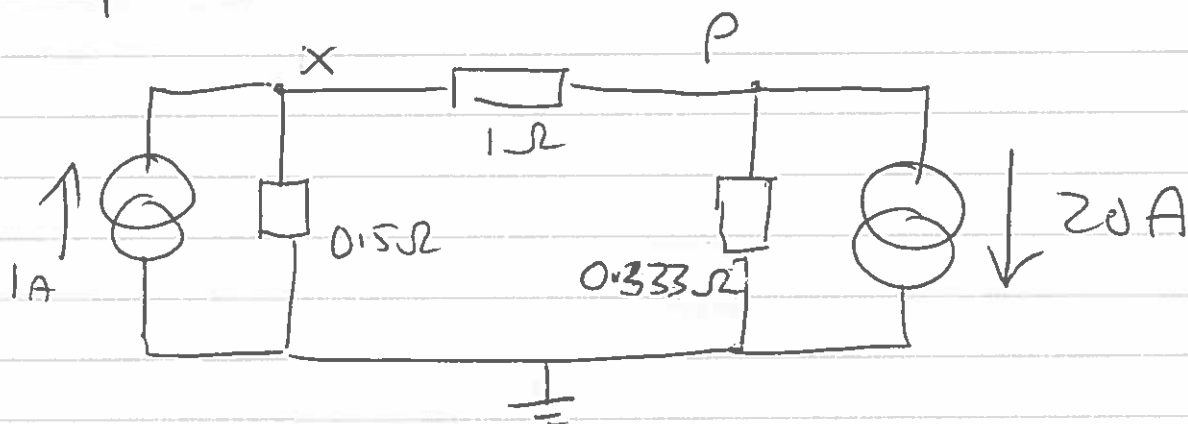In parallel we combine sources & resistors




Eliminate  $V_a$  to get

$$V_{out} = -g_m \frac{R_2 R_D}{R_1 + R_2} V_{in}$$


$$\text{Gain } G = \frac{V_{out}}{V_{in}} = -g_m \frac{R_2 R_D}{R_1 + R_2}$$

The gain is negative  $\Rightarrow$  inverting (see AC section)

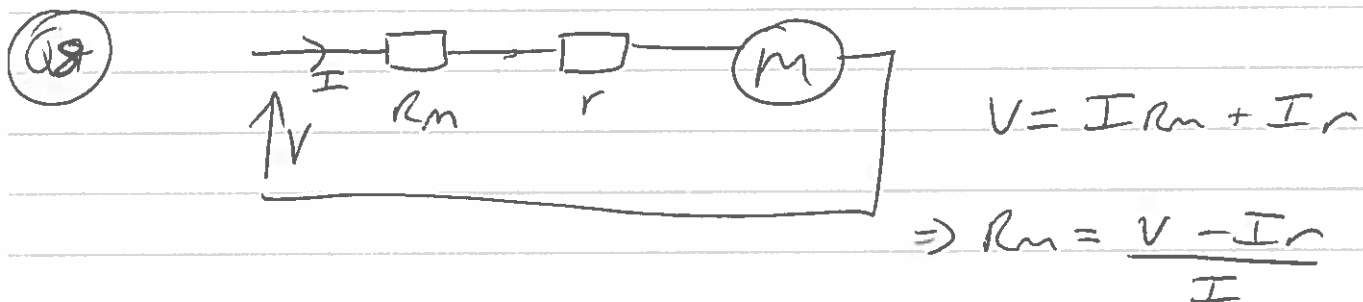$g_m$  must have units of  $\Omega^{-1}$  (Siemens)  
it is a Transconductance



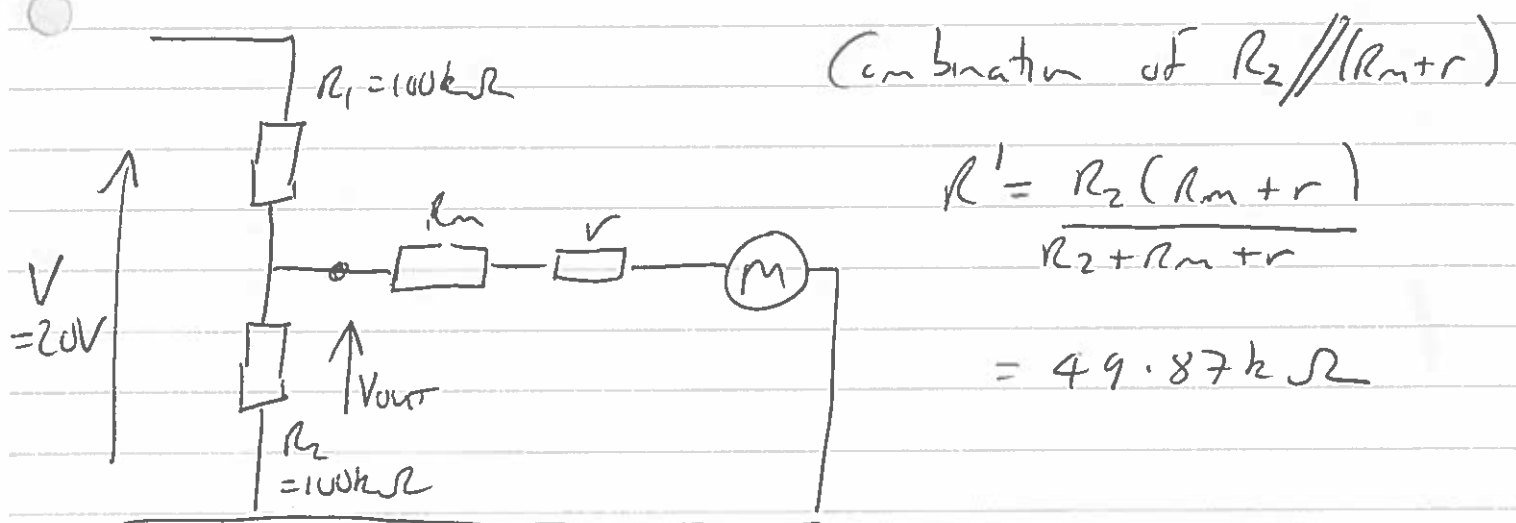On 10V range  $V = 10V$  &  $I = 100\mu A$   
Full scale  $\Rightarrow R_m = 99.5k\Omega$



P. Divider (From first problem)  $\Rightarrow V_{out} = \frac{R' V}{R_1 + R'} = \frac{49.87k \times 20}{100k + 49.87k} = 6.66V$

With no meter  $V_{out} = 10V$  here can see effect of meter.