

**Part 1A Paper 3 : Electrical and Information Engineering**  
**DIGITAL CIRCUITS AND INFORMATION PROCESSING**  
**EXAMPLES PAPER 1**

\* Harder questions.      † Straightforward questions.

- † 1. Complete the truth tables for the logic circuits in Figures 1 and 2.

 


Figure 1:

Inputs		Table for Figure 1				
A	B	$\bar{A}$	$\bar{A}.B$			X
0	0					
0	1					
1	0					
1	1					

 


Figure 2:

Inputs		Table for Figure 2				
A	B	$\bar{A}$	$\overline{A+B}$			Y
0	0					
0	1					
1	0					
1	1					

- † 2. Find the state of inputs  $A$ ,  $B$  and  $C$  for which the circuit of Figure 3 has output  $Z$  at logic 1.

 


Figure 3:

3. The NMOS field-effect transistor with characteristics shown in Figure 4(b) is connected into the inverter circuit shown in Figure 4(a).

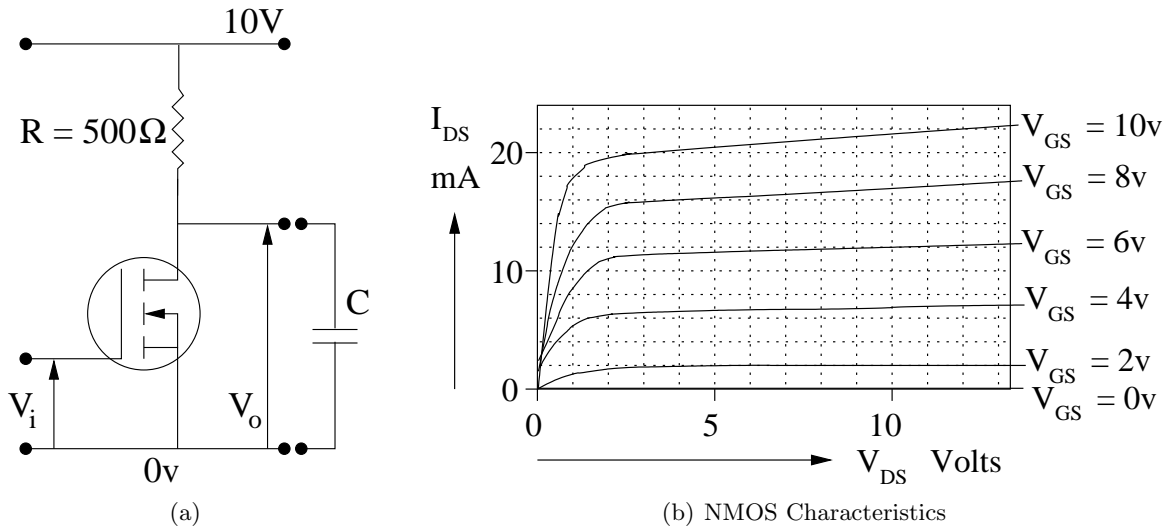


Figure 4:

- (a) Draw a load line on Figure 4(b) and determine the output voltage  $V_o$  corresponding to input voltages of 0V and +10V.
- (b) Calculate the power dissipated in the  $500\Omega$  resistor and the transistor for each input voltage.

- (c) The capacitor  $C$  is now connected to the output of the circuit, as shown in the figure.  $V_i$  is initially 10V. At time  $t = 0$ ,  $V_i$  falls to 0V, switching the transistor off. Show that  $V_o$  as a function of time is  $10 - 9 \exp(-t/(CR))$ . If  $C = 40\text{pF}$ , find the time for  $V_o$  to rise from 1V to 8V.

4. Figure 5(a) shows a NMOS gate where a second transistor  $T_1$  replaces the load resistor. The characteristics of  $T_1$  are identical to that shown in Figure 4(b). Using the fact that  $V_{DS} = V_{GS}$  for this transistor, construct a graph showing the relationship between  $V_{DS}$  and  $I_{DS}$  for  $T_1$ .

Show that  $T_1$  is equivalent to a voltage drop  $V_1$  in series with a resistor  $R_1$ , so that the circuits of Figures 5(a) and 5(b) are identical. Find  $V_1$  and  $R_1$ .

 


Figure 5:

Draw a new load line on Figure 4(b) to represent the possible working points of  $T_2$ . Assume  $V_{DD} = 10\text{V}$ , and hence find the output voltage  $X$  corresponding to input voltages of 2V and 10V.

The table shown in Figure 5(c) summarises the operation of the circuit; complete the second line.

- † 5. Figures 6(a) and 6(b) show simple extensions of the inverter circuit of Figure 5(a). By completing the tables,

Inputs		Table for (a)		
$A$	$B$	$T_2$	$T_3$	$X$
0	0			
0	1			
1	0			
1	1			

Inputs		Table for (b)		
$A$	$B$	$T_4$	$T_5$	$Y$
0	0			
0	1			
1	0			
1	1			

determine what function the outputs  $X$  and  $Y$  are of the inputs  $A$  and  $B$ .

 


Figure 6:

- \* 6. A CMOS (Complementary MOS) inverter circuit is shown in Figure 7(a) in which the  $500\Omega$  resistor of Figure 4(a) has been replaced by a PMOS transistor  $T_1$  with characteristics shown in Figure 7(b). The characteristic of the NMOS transistor is repeated as Figure 7(c).
- Determine the output voltages  $V_o$  corresponding to input voltages  $V_i$  of 0V and 10V (Low and High inputs).
  - Check that the power dissipated in each transistor for high and low inputs is negligible.
  - If, due to a faulty lead, the input is floating and becomes +4V, determine  $V_o$ , the power dissipated in each transistor, and the power taken from the supply.

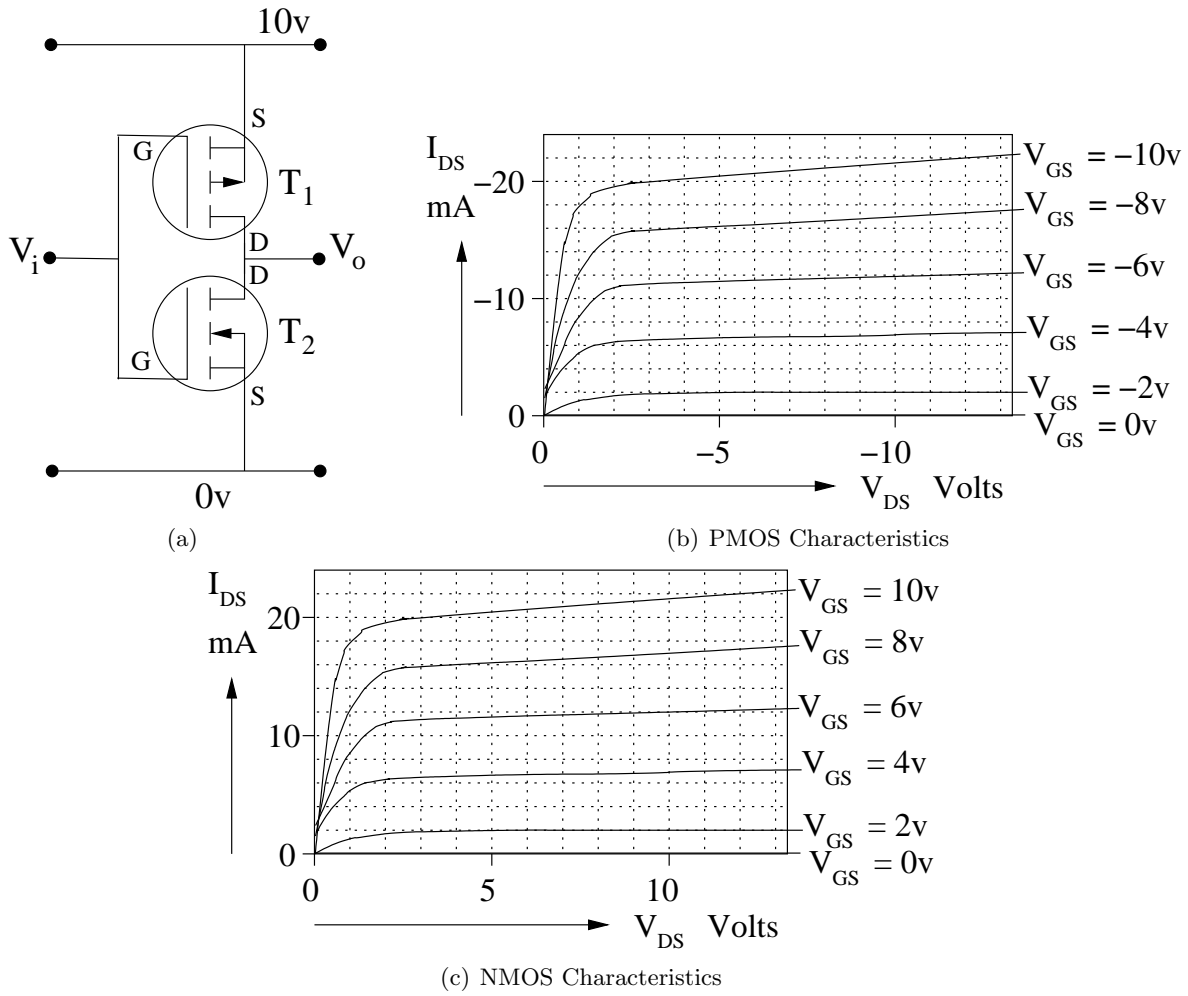


Figure 7:

7. Use Boolean algebra to prove the following identities:

$$A.B.C + A.B.\overline{C} = A.B$$

$$A.(\overline{A} + B) = A.B$$

$$A.B + \overline{A}.C = (A + C).(\overline{A} + B)$$

$$(A + C).(A + D).(B + C).(B + D) = A.B + C.D$$

- † 8. The circuit of Figure 8 does not make efficient use of logic gates. Write a Boolean expression for  $Z$  and hence show how  $Z$  can be realised more simply.

9. A logic 'voter' circuit has four inputs  $A, B, C, D$  and one output  $V$ . The output is to be logic 1 if any three or all four inputs are at logic 1. Design a circuit using AND and OR gates to satisfy this requirement.

 


Figure 8:

\* 10. Devise circuits to solve question 9 if

- (a) NAND gates only;
- (b) NOR gates only are to be used.

HINT for part (b): consider when no output is wanted from the circuit and write a new Boolean expression. Then use de Morgan's theorem.

11. Following the examples on pages 67 and 68 of handout 1, write a VHDL definition of an OR gate.

Using this definition, and the gates defined in the handout, produce a VHDL description of the circuit shown in Figure 3.

R V Penty  
Lent 2019

Revision tripsos questions: 2012 Paper 3 Question 6  
2014 Paper 3 Question 6  
2016 Paper 3 Question 6  
2017 Paper 3 Question 6 .

## ANSWERS

1.

Inputs		Outputs	
$A$	$B$	$X$	$Y$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

2.  $Z = 1$  for  $ABC$  in the states 000, 001 and 101.

3. 10V, 1V, 0mW, 0mW, 162mW, 18mW, 30.1ns.

4. 1.5V, 395 $\Omega$ , 8V, 1.2V, 1 ON 0.

5. NAND, NOR.

6. 10V, 0V, approx 9V, 63mW, 7mW, 70mW.

8.  $Z = A + B$

9.  $V = A.B.C + A.B.D + A.C.D + B.C.D$

10.

$$V = \overline{\overline{(A.B.C).(\overline{A.B.D}).(\overline{A.C.D}).(\overline{B.C.D})}}$$

$$V = \overline{\overline{(A+B) + (A+C) + (A+D) + (B+C) + (B+D) + (C+D)}}$$