

# 1A Analyser of cct + dev Ex #3 CRB0

Q1 a) DC  $\rightarrow$  no C + C  $\equiv$  open ckt

$$\Rightarrow \text{input } V_{in} \Rightarrow \text{pot divider } \frac{R_{in}}{R_s + R_{in}}$$

$$\Rightarrow V' = V_{in} \frac{R_{in}}{R_s + R_{in}} \quad R_{in} = V_{in} \quad \text{or } R_{in} = (M\Omega) \gg 1k\Omega$$

$$\text{at output } V_{out} = 100 V' \frac{R_c}{R_{out} + R_c} = 100 V_{in} \frac{9k}{1k + 9k} = 90 V_{in}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = 90$$

b) Include  $C_L // R_c = \frac{R_c \frac{1}{j\omega C_L}}{R_c + \frac{1}{j\omega C_L}} \times \frac{j\omega C_L}{j\omega C_L} = \frac{R_c}{1 + j\omega C_L R_c}$

From Midband (a)  $V_{out} = 100 V_{in} \frac{R_c}{R_{out} + R_c}$

Replace  $R_c$  with  $R_c // R_c$

$$\Rightarrow \frac{V_{in}}{V_{out}} = 100 \frac{R_c / (1 + j\omega C_L R_c)}{R_{out} + R_c / (1 + j\omega C_L R_c)} \times \frac{1 + j\omega C_L R_c}{1 + j\omega C_L R_c}$$

$$= \frac{100 R_c}{R_c + (1 + j\omega C_L R_c) R_{out}} \quad \left( \frac{A + jB}{C + jD} \right) \Rightarrow \text{e = D}$$

$$\Rightarrow R_c + R_{out} = \omega C_L R_c R_{out} \Rightarrow f = \frac{R_c + R_{out}}{2\pi C_L R_c R_{out}} = 980 \text{ Hz}$$

(1)

c) switch to AC & ignore  $C_L$  ( $\approx$  open ckt)

$$\Rightarrow V_{out} = 100V_{in} \frac{R_C}{R_{out} + 1/j\omega C + R_L} \times \frac{j\omega C}{j\omega C}$$

$$= \frac{j\omega C R_L}{1 + j\omega C (R_{out} + R_L)}$$

$$\Rightarrow 3dB \text{ when } 1 = \omega C (R_{out} + R_L)$$

$$(1/\sqrt{2}) \Rightarrow f = \frac{1}{2\pi C (R_{out} + R_L)} = 1.6Hz$$

d) Power gain defined as:  $\left| \frac{V_{out}}{V_{in}} \right|^2 \times \frac{R_{in}}{R_L}$


$$\text{in decibels} = 10 \log_{10} \left[ \left| \frac{V_{out}}{V_{in}} \right|^2 \frac{R_{in}}{R_L} \right]$$

$$= 10 \log_{10} (900,000) = 59.5dB$$

e) In dB, add power gain

$$\Rightarrow G = 40 - 4 + 59.5 = 95.5dB$$

Q2) Multi-stage cascaded amplifier

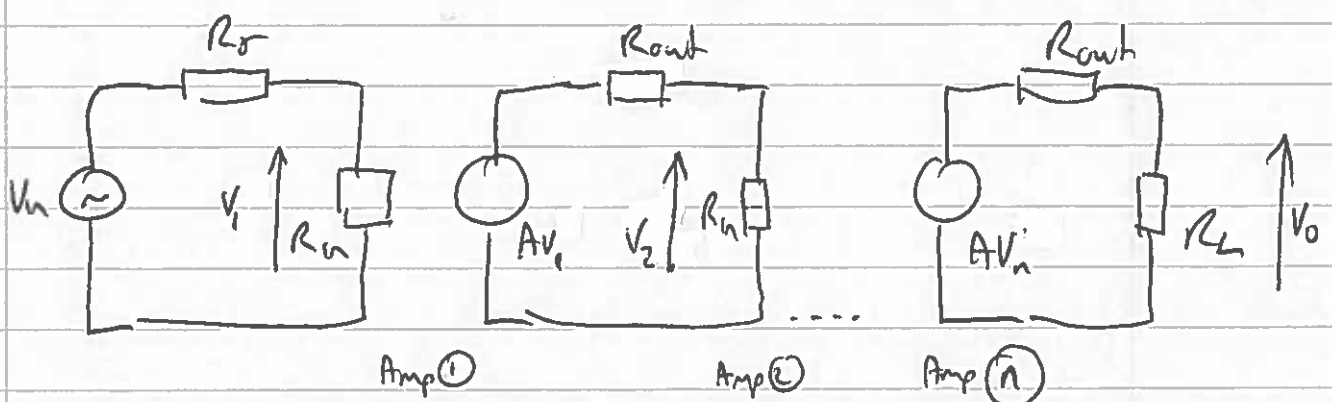

(2)

At input  $V' = \frac{R_{in}}{R_s + R_{in}} V_{in}$

1st amp output to 2nd amp input

$$V_2 = A_{V1} \frac{R_{in}}{R_{in} + R_{out}}$$

This then repeats  $n-1$  times till the last ( $n^{th}$ ) stage output

$$V_o = \frac{R_L}{R_{out} + R_L} A_{Vn}$$

$\Rightarrow$  Total gain of the cascade

$$G = \frac{V_o}{V_{in}} = \left( \frac{R_{in}}{R_s + R_{in}} \right) \times \left( \frac{A R_{in}}{R_{in} + R_{out}} \right)^{n-1} \times \frac{A R_L}{R_{out} + R_L}$$

Input voltage  $V_{in} = 1 \text{ mV}_{p-p} = 0.5 \text{ mV}_p$

$V_o$  required  $\approx 1 \text{ V}_p$   $20 \text{ dB} \rightarrow A = 12.59$  per stage

$$\Rightarrow \text{Gain} = \frac{1}{0.5 \times 10^{-3}} = 2000$$

$$\Rightarrow 2000 = \left( \frac{100 \text{ k}}{10 \text{ k} + 100 \text{ k}} \right) \left( \frac{100 \text{ k} \times 12.59}{100 \text{ k} + 1 \text{ k}} \right)^{n-1} \left( \frac{12.59 \times 100 \text{ k}}{1 \text{ k} + 100 \text{ k}} \right)$$

$$\approx 0.91 \times (12.47)^{n-1} \times (12.47)$$


$$(12.47)^n = \frac{2000}{0.91} = 2198 \Rightarrow n = 3.05$$

(3)

3 stages will be ok as  
can add a bit of extra gain to 1 stage.

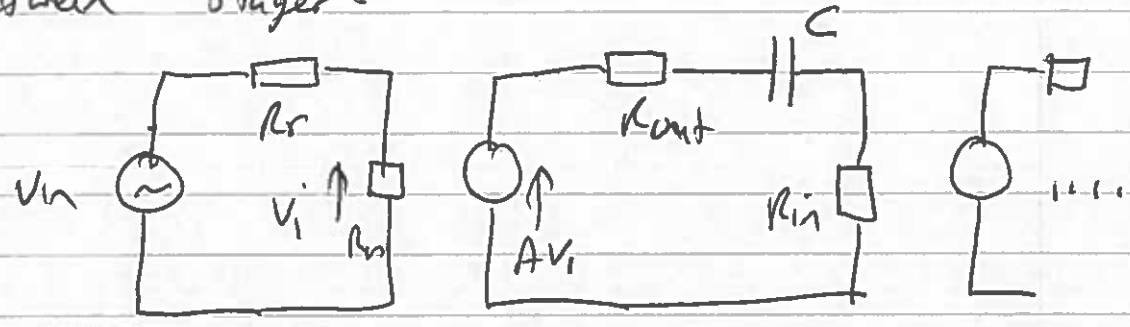Q2  
cont


Each stage has its own DC biasing as we do not want DC currents between stages, here we add a capacitor between each stage to block ~~the~~ DC and allow AC signals to pass between stages.



This is in fact the same situation as in Q1 part (c) where  $C$  is acting as a ~~decoupling~~ decoupling capacitor between each stage, but  $R_s = R_{in}$ .

From  $\Rightarrow f = \frac{1}{2\pi C(R_{out} + R_{in})}$   
 Q1 (c)  $\Rightarrow f = 100 \text{ Hz} \Rightarrow C = \frac{1}{2\pi \times 100 \times (100 \times 10^3 + 1 \times 10^3)}$   
 $= 1.58 \times 10^{-8} \text{ F}$   
 $(15.8 \text{ nF})$

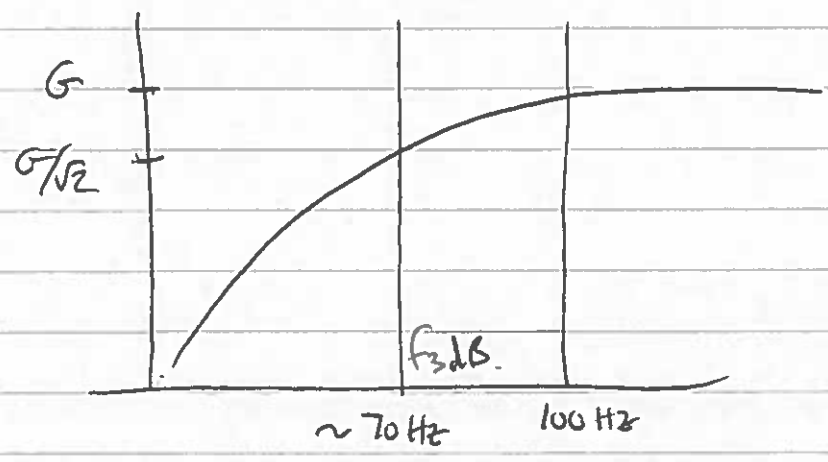In reality we would probably choose a 3dB frequency less than 100 Hz to reduce the effect of the  $1/\sqrt{2}$  attenuation at the 3dB freq.



3. Use  $R = \frac{\rho l}{A}$ ,  $R = \frac{\rho \times 100 \times 10^{-6}}{10 \times 10^{-6} \times 1 \times 10^{-6}} = 10^7 \rho$


Copper,  $\rho = 1.7 \times 10^{-8} \Omega \text{m} \Rightarrow R = 0.17 \Omega$

Current,  $I = V/R = \frac{1 \text{ V}}{0.17 \Omega} = 5.88 \text{ A}$


Power,  $P = VI = 5.88 \text{ W}$ .

4. Draw the load-line, using the relationship  $V_D = 5 - 1000I_D$ .  $\Rightarrow I_D = 5 \times 10^{-3} - V_D/1000$ ,  
or  $I_D \text{ (mA)} = 5 - V_D \text{ (mV)}$  [this is the upper line shown below]. This intercepts the diode curve at  $I_D = 4.5$   
mA,  $V_D = 0.475 \text{ V}$ .


(a)

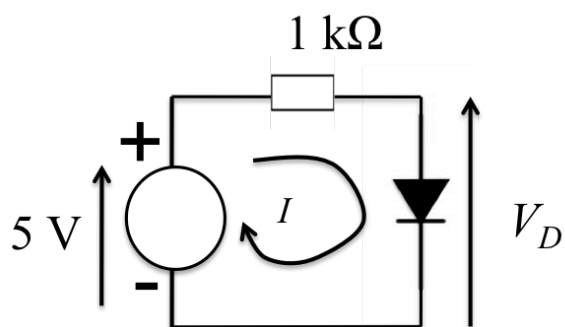

(b)

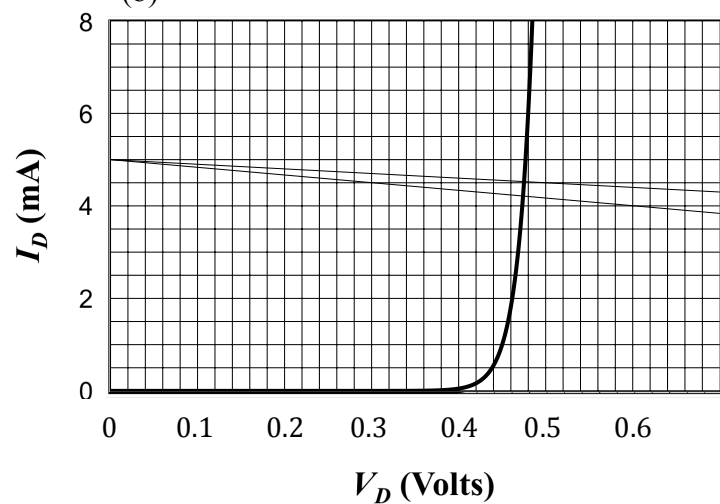

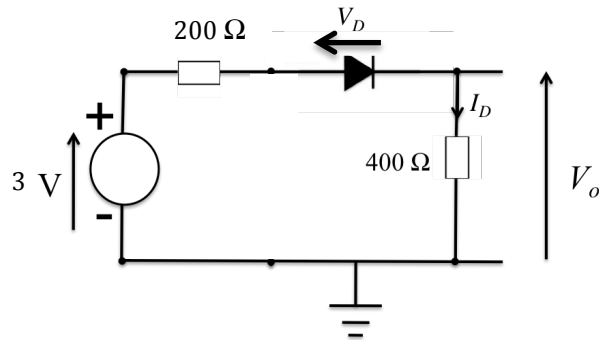5. Replace the battery and the  $600\ \Omega$  and  $300\ \Omega$  resistors with their Thevenin equivalent to simplify the circuit:



$$V_o = 400I_D$$

Applying Kirchhoff's voltage law around the loop, we obtain:

$$3 - 200I_D - V_D - 400I_D = 0 \quad \dots\dots\dots \text{there will be a voltage drop across the diode.}$$

$$\Rightarrow I_D = \frac{3}{600} - \frac{V_D}{600}$$


$$\text{From which we find that } I_D \text{ (mA)} = 5 - 1.66V_D \text{ (mV)}$$

This is the lower line on the diode curve, from which we find that at  $I_D = 4.25\text{ mA}$ ,  $V_D = 0.4\text{ V}$ .

The output voltage,  $V_o = 400I_D = 1.7\text{ V}$ .

## FET Amplifiers

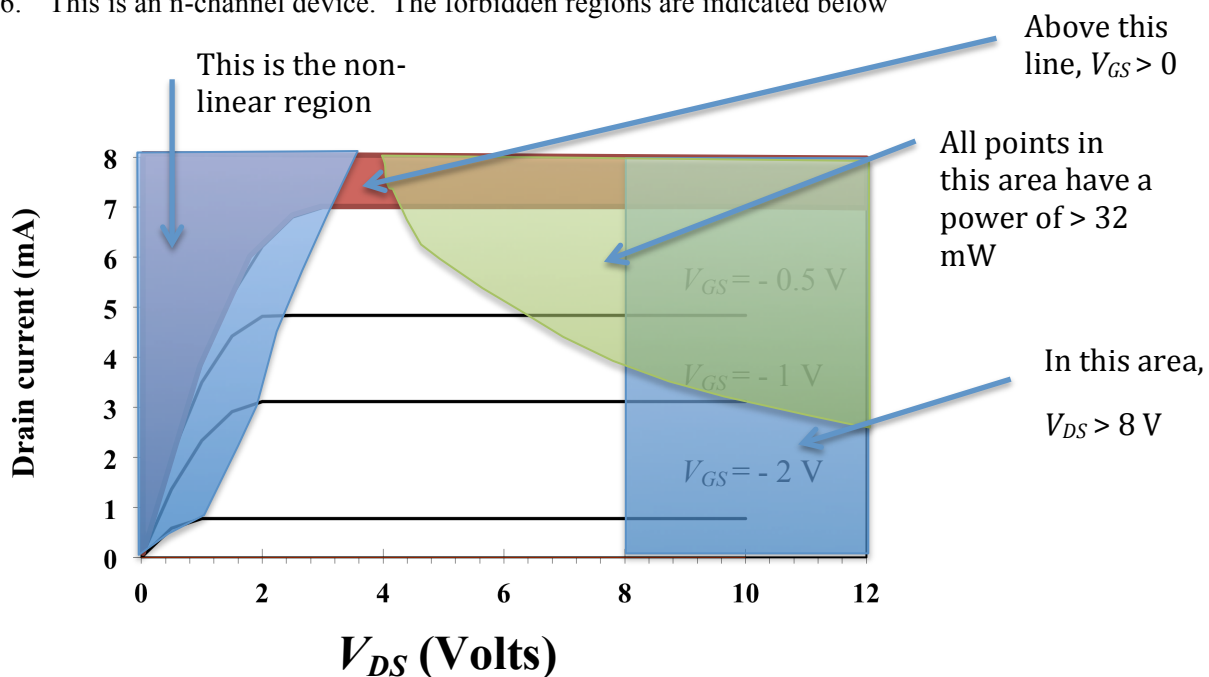
6. This is an n-channel device. The forbidden regions are indicated below



6 7. The operating point is P, where  $V_{DS} = 5 \text{ V}$ ,  $V_{GS} = -0.5 \text{ V}$ ,  $I_D = 4.8 \text{ mA}$ .

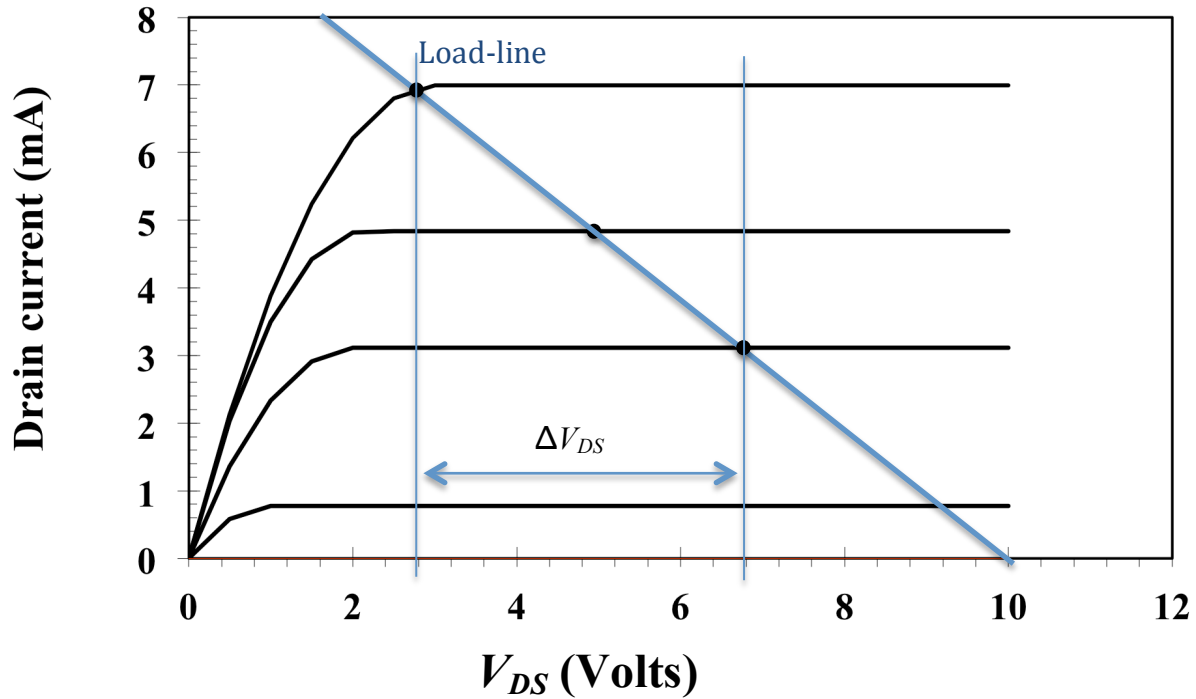(i) The voltage across  $R = 10 \text{ V} - V_{DS} = 5 \text{ V}$ .

$\Rightarrow R = 5 \text{ V} / 4.8 \text{ mA} = 1.042 \text{ k}\Omega$ .



(ii) From the load-line, when  $V_{GS}$  changes between 0 & -1 V, the load-line intercepts move to  $V_{DS} = \sim 2.8 \text{ V}$  and 6.8 V. Therefore, the change in  $V_{DS}$  is 4 V. The gain is (change in  $V_{DS}$ ) / (change in  $V_{GS}$ ) = -4.

7 8. The operating point is the same as before, so the voltage across  $R_2$  is 0.5 V ( $V_{GS}$ ).

$\Rightarrow R_2 = 0.5 \text{ V} / 4.8 \text{ mA} = 104.2 \Omega$ .

The voltage across  $R_1$  is  $10 \text{ V} - 5 \text{ V} - 0.5 \text{ V} = 4.5 \text{ V}$ ,  $\Rightarrow R_1 = 4.5 \text{ V} / 4.8 \text{ mA} = 937.5 \Omega$ .