

Part 1A Paper 4: Electrical and Information Engineering,

ANALYSIS OF CIRCUITS EXAMPLES PAPER 4

Questions containing material of tripos standard are marked *.

Small-signal models

1. (i) For the MOSFET with the characteristics shown in Fig. 1 below, graphically estimate the values of the small-signal parameters g_m and r_d at the operating point, P. Is it an enhancement or depletion mode device?

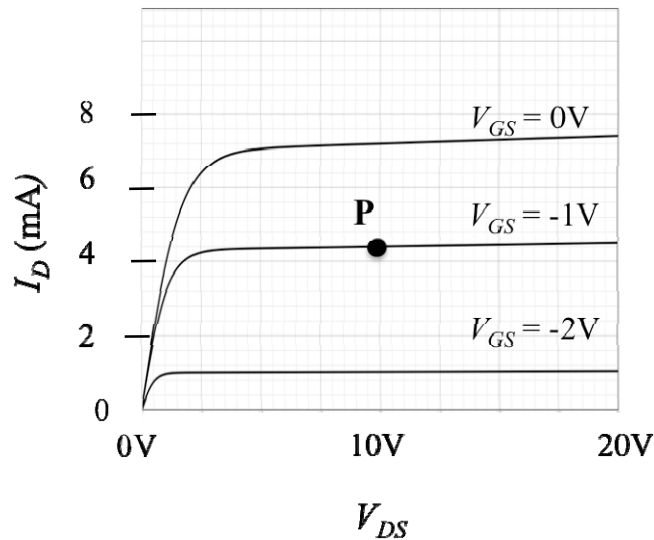


Fig. 1

- (ii) For the circuit in Fig. 2(a), calculate the value of the components in the circuit for it to be biased at point P, assuming $V_{DD} = 20$ V. The small-signal model of the circuit in Fig. 2(a) is shown in Fig. 2(b). What do R_1 , R_2 & R_3 represent?

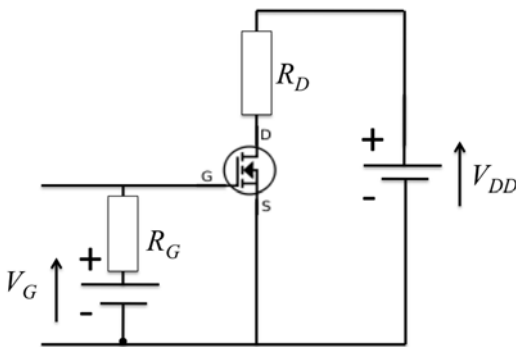


Fig. 2(a)

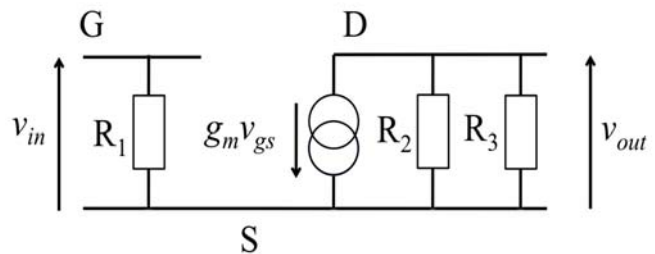


Fig. 2(b)

2. A FET has small-signal parameters $g_m = 4 \text{ mS}$ and $r_d = 10 \text{ k}\Omega$ at the following operating point: $V_{DS} = 8 \text{ V}$, $I_D = 2.5 \text{ mA}$, $V_{GS} = 2 \text{ V}$.

Design a common source amplifier circuit using this FET, with a +30 V power supply (V_{DD}). The input is connected to the gate and a bias circuit consisting of a potential divider constructed between V_{DD} and ground.

- Sketch the circuit diagram of this amplifier labeling all of the components required.
- Determine the value of resistor between the drain and V_{DD} and the ratio of values of the potential divider resistors in the gate bias circuit that will enable the operating point to be achieved.
- Draw the small-signal equivalent circuit of your design and use it to calculate the small-signal voltage gain of the circuit.
- If the input resistance of the amplifier must be greater than $100 \text{ k}\Omega$, determine values of the potential divider resistors that satisfy this requirement.

3. *The circuit shown in Fig. 3 is known as a source-follower and is a key part of the IEP radio design. If $R_1 = 2 \text{ M}\Omega$ and the FET has small-signal parameters $g_m = 5 \text{ mS}$, $r_d = 50 \text{ k}\Omega$, and the operating point for the FET is set at $V_{DS} = 7 \text{ V}$, $I_D = 2.6 \text{ mA}$, $V_{GS} = -3 \text{ V}$.

- Calculate values for R_2 & R_3 that will enable the desired operating point to be achieved.
- Draw the small-signal equivalent circuit.
- Using the small-signal circuit, calculate the circuit's input resistance, output resistance (be careful!) and voltage gain.

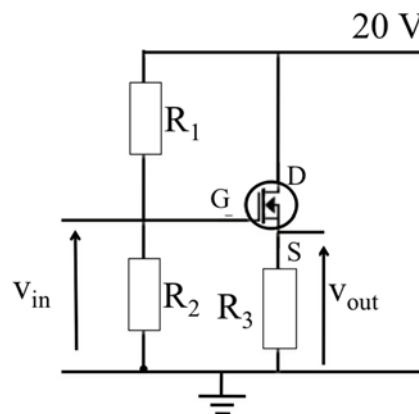


Fig. 3

4. A simple FET amplifier is shown below in Fig. 4. The small-signal parameters for the FET are $g_m = 4 \text{ mS}$ and $r_d = 10 \text{ k}\Omega$. What value of output coupling capacitor, C , is needed between the drain and the load, assuming that the load resistance is 500Ω , and the voltage can drop to 70% ($1/\sqrt{2}$) of its maximum value at 20 Hz? How many dB lower is the gain at this frequency than at mid-band?

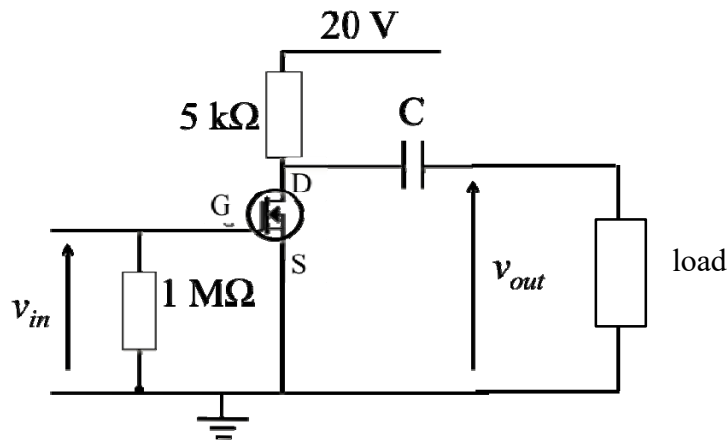


Fig. 4

5. *In the amplifier circuit shown in Fig. 5, the FET has a mutual conductance, $g_m = 4 \text{ mS}$ and an effectively infinite drain resistance, r_d . The component values are $R_1 = 20 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$ and $C = 4 \mu\text{F}$.

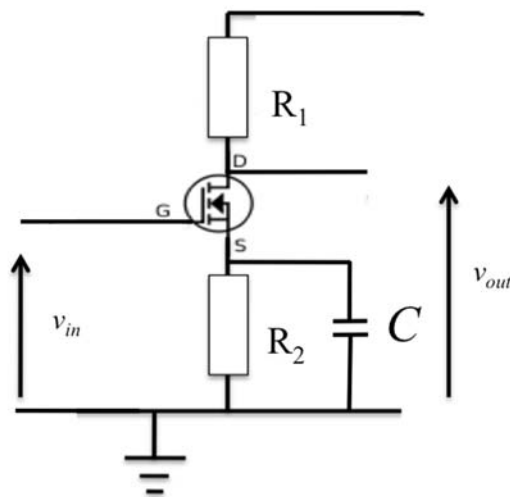


Fig. 5

Derive an expression for the gain without C in place. Repeat the derivation to include C and comment on the role of R_2 in the circuit. Calculate the gain at frequencies of 1.59 Hz, 159 Hz and 15.9 kHz and sketch a Bode plot of the gain versus angular frequency. Is the circuit complete?

Op-Amps

- 6) What is the op-amp circuit shown in Figure 6 ? Derive an expression for its gain given that the op-amp is ideal.

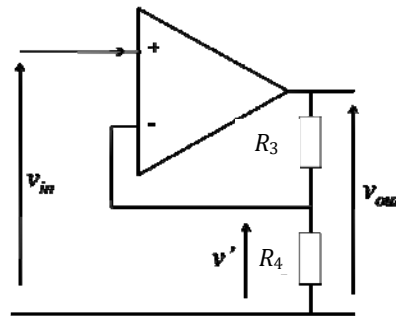


Fig. 6

7. Fig. 7 shows the circuit diagram of *summing amplifier*. Assuming an ideal op-amp, show that the output voltage, v_{out} is given by:

$$v_{out} = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2\right)$$

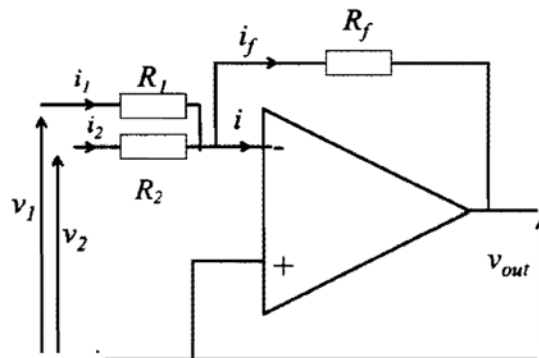


Fig. 7

- (a) An audio summing circuit is required to produce an output of $-(200v_1 + 40v_2)$. If $R_f = 100 \text{ k}\Omega$, what values are required for R_1 & R_2 , given that the signal sources providing v_1 & v_2 each have an internal output impedance of 200Ω ?
- (b) The op-amp is powered from a bipolar voltage supply that delivers $+V$ and $-V$ relative to earth. If v_1 & v_2 have peak amplitudes 10 mV and 50 mV , respectively, determine the minimum power supply voltages required for the circuit to work correctly.

8. The circuit in Fig. 8 is known as a *Transimpedance Amplifier*. It is commonly used to amplify a very small ac current, i and produce a proportional voltage output v_{out} .

(a) Derive an expression for the output voltage as a function of the input current (the transimpedance).

(b) The resistor, R is often set to a large value ($\sim 10 \text{ M}\Omega$), however it will also have stray capacitance (in parallel with R). If the value of this stray capacitance is estimated to be 2 pF , calculate the resulting -3dB frequency for the circuit.

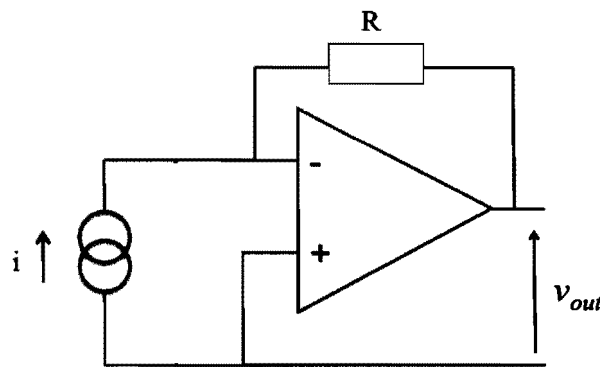


Fig. 8

Answers:

1. (i) $\sim 4.6 \text{ mS}$, $\sim 40 \text{ k}\Omega$; (ii) $V_G = -1\text{V}$, $R_G \sim 1 \text{ M}\Omega$, $R_D = 2.5 \text{ k}\Omega$, $R_1 = R_G$, $R_2 = r_d$, $R_3 = R_D$.

2. (a) $8.8 \text{ k}\Omega$, 14, (b) -18.7 (c) $1.5 \text{ M}\Omega$ gate to the power supply, $107 \text{ k}\Omega$ gate to ground.

3. (a) $R_3 = 5 \text{ k}\Omega$, $R_1 = R_2 = 2 \text{ M}\Omega$ (c) gain = 0.958, $R_{in} = 1 \text{ M}\Omega$, $R_{out} = 192 \Omega$.

4. $2.08 \mu\text{F}$; 3dB.

5. $\frac{v_{out}}{v_{in}} = -\frac{g_m R_1}{1 + g_m R_2}$, $\frac{v_{out}}{v_{in}} = -\frac{g_m R_1 (1 + j\omega C R_2)}{1 + g_m R_2 + j\omega C R_2}$, -9, -53, -80

6. Non-inverting amplifier, $\frac{v_{out}}{v_{in}} = \frac{R_3 + R_4}{R_4}$

7. (a) $R_1 = 300 \Omega$, $R_2 = 2300 \Omega$; Power supplies should be at least +4V and -4V

8. (a) $-R$; (b) 8 kHz.