

①

# 1A Linear Circuits and Devices - Solutions to Example Paper

AC Power

1

$$i) \quad \tilde{I} = \frac{\tilde{V}}{Z} = \frac{240 \angle 0}{48 + j36} = \frac{240 \angle 0}{60 \angle 36.9^\circ} = \underline{4 \angle -36.9^\circ \text{ A}}$$

$$ii) \quad \text{Power factor} = \cos \phi = \cos(36.9^\circ) = \underline{0.8 \text{ lagging}}$$

(lagging because  $\tilde{I}$  lags  $\tilde{V}$  since load is R-L)

$$iii) \quad P = VI \cos \phi = 240 \times 4 \times 0.8 = \underline{768 \text{ W}}$$


$$iv) \quad Q = VI \sin \phi = 240 \times 4 \times \sin(36.9^\circ) = \underline{576 \text{ VAR}}$$

Notice that  $Q$  is positive, consistent with inductors consuming reactive power.

$$|\tilde{I}| = 4 \text{ A} \quad P = I^2 R = 4^2 \times 48 = \underline{768 \text{ W}}$$

$$Q = I^2 X_L = 4^2 \times 36 = \underline{576 \text{ VAR}}$$

2/

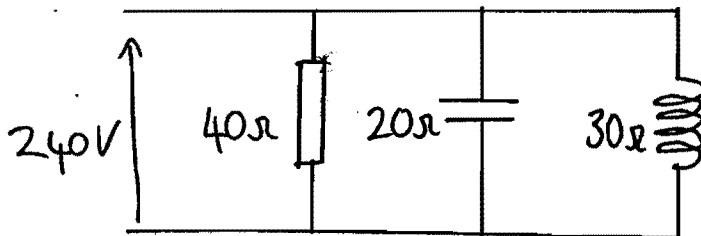

$$i) \quad \frac{1}{Z} = \frac{1}{R} + \frac{1}{jX_L} + \frac{1}{-jX_C}$$

$$= \frac{1}{40} + j \left( \frac{1}{20} - \frac{1}{30} \right)$$

$$= 0.025 + j0.016\bar{6} = 0.0300 \angle 33.7^\circ$$

(2)

$$\therefore \underline{Z = 33.3 \angle -33.7^\circ \Omega}$$

$$\tilde{I} = \frac{\tilde{V}}{Z} = \frac{240 \angle 0}{33.3 \angle -33.7^\circ} = \underline{7.21 \angle 33.7^\circ \text{ A}}$$

ii) Power factor =  $\cos(-33.7^\circ) = \underline{0.832 \text{ leading}}$

(leading because  $\tilde{I}$  leads  $\tilde{V}$ )

$$P = VI \cos \phi = 240 \times 7.21 \times \cos(-33.7^\circ) = \underline{1.44 \text{ kW}}$$


$$Q = VI \sin \phi = 240 \times 7.21 \times \sin(-33.7^\circ) = \underline{-960 \text{ VAR}}$$

Much easier - use the fact that only the resistor consumes  $P$ , only the capacitor and inductor consume  $Q$

$$P = \frac{V^2}{R} = \frac{240^2}{40} = \underline{1.44 \text{ kW}}$$

$$Q = \frac{V^2}{X_L} - \frac{V^2}{X_C} = 240^2 \left( \frac{1}{30} - \frac{1}{20} \right) = \underline{-960 \text{ VAR}}$$

3/1)

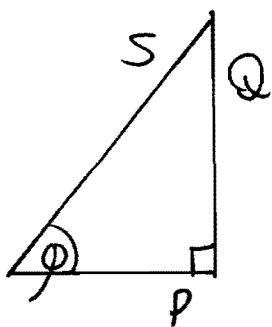

Load 1

$$S = 250 \text{ kVA}, \cos \phi = 0.5 \text{ lagging}$$

$$\text{From power triangle, } P = S \cos \phi = 250 \times 0.5 = \underline{125 \text{ kW}}$$

$$Q = (S^2 - P^2)^{1/2} = (250^2 - 125^2)^{1/2} = \underline{217 \text{ kVAR}}$$

Load 2  $P = 180 \text{ kW}$ ,  $\cos\phi = 0.8$  leading

From power triangle  $P = S \cos\phi \Rightarrow S = \frac{P}{\cos\phi} = \frac{180}{0.8} = \underline{225 \text{ kVA}}$ .

$$Q = (S^2 - P^2)^{1/2} = (180^2 - 225^2)^{1/2} = \underline{-135 \text{ kVAR}}$$

(Notice  $Q$  is -ve, since the power factor is quoted as leading).

Load 3  $S = 300 \text{ kVA}$ ,  $Q = 100 \text{ kVAR}$

From power triangle  $P = (S^2 - Q^2)^{1/2} = (300^2 - 100^2)^{1/2} = \underline{283 \text{ kW}}$

$$\text{Power factor} = \cos\phi = \frac{P}{S} = \frac{283}{300} = \underline{0.943 \text{ lagging.}}$$

(Power factor is lagging because reactive power is +ve).

ii) By conservation of real and reactive power:-

$$P_T = P_1 + P_2 + P_3 = 125 + 180 + 283 = \underline{588 \text{ kW}}$$

$$Q_T = Q_1 + Q_2 + Q_3 = 217 - 135 + 100 = \underline{182 \text{ kVAR}}$$

From power triangle, overall power factor  $\cos\phi_T = \frac{P_T}{S_T}$

$$\text{Total apparent power, } S_T = (P_T^2 + Q_T^2)^{1/2} = (588^2 + 182^2)^{1/2} = 616 \text{ kVA}$$

$$\therefore \cos\phi_T = \frac{588}{616} = \underline{0.955 \text{ lagging}}$$

(Overall power factor quoted as lagging since overall reactive power turned out to be +ve).

④

For unity power factor,  $\cos\phi = 1 \Rightarrow \phi = 0, \Rightarrow Q = 0$

$\therefore$  Capacitor must generate 182 kVAR

$$\text{Capacitor VARs} = \frac{V^2}{X_c} = \frac{V^2}{1/\omega C} = \omega C V^2 = 2\pi f C V^2$$

$$\therefore 2\pi \times 50 \times C \times (2000)^2 = 182 \times 10^3$$

$$\underline{C = 145 \mu\text{F}}$$

4/ i) a)  $S = 1.2 \text{ kVA}$ ,  $\cos\phi = 0.7$  lagging.

From power triangle  $P = S \cos\phi = 1.2 \times 0.7 = \underline{840 \text{ W}}$

$$Q = (S^2 - P^2)^{1/2} = (1200^2 - 840^2)^{1/2} = \underline{857 \text{ VAR}}$$

b)  $P = 4 \times 100 \text{ W} = \underline{400 \text{ W}}$   $\underline{Q = 0 \text{ VAR}}$  since  $\cos\phi = 1$

c)  $S = VI = 240 \times 3 = 720 \text{ VA}$  ;  $\cos\phi = 0.8$  leading

$$P = S \cos\phi = 720 \times 0.8 = \underline{576 \text{ W}}$$

$$Q = (S^2 - P^2)^{1/2} = (720^2 - 576^2)^{1/2} = \underline{-432 \text{ VAR}}$$

d)  $|\tilde{I}| = \frac{|\tilde{V}|}{|Z|} = \frac{240}{(50^2 + 20^2)^{1/2}} = 4.46 \text{ A}$

$$P = I^2 R = 4.46^2 \times 50 = \underline{993 \text{ W}}$$

$$Q = I^2 X_L = 4.46^2 \times 20 = \underline{397 \text{ VAR}}$$

(Note use of  $I^2 R$ ,  $I^2 X$  for series-connected circuit)

(5)

ii) By conservation of P and Q:

$$P_T = P_1 + P_2 + P_3 + P_4 = 840 + 400 + 576 + 993 = \underline{\underline{2809 \text{ W}}}$$


$$Q_T = Q_1 + Q_2 + Q_3 + Q_4 = 857 + 0 + (-432) + 397 = \underline{\underline{822 \text{ VAR}}}$$

iii) From power triangle  $S_T = (P_T^2 + Q_T^2)^{1/2} = (2809^2 + 822^2)^{1/2} = \underline{\underline{2927 \text{ VA}}}$

$$S_T = V I_T \Rightarrow 2927 = 240 I_T \Rightarrow \underline{\underline{I_T = 12.2 \text{ A}}}$$

$$\text{Input power factor } \cos \phi_T = \frac{P_T}{S_T} = \frac{2809}{2927} = \underline{\underline{0.960 \text{ lagging}}}$$

5/

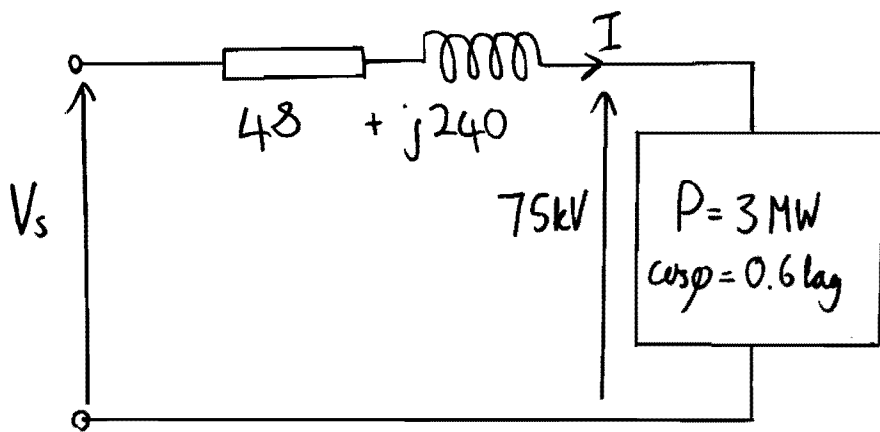

i) From power triangle  $S = \frac{P}{\cos \phi} = \frac{3}{0.6} = \underline{\underline{5 \text{ MVA}}}$

$$Q = (S^2 - P^2)^{1/2} = (5^2 - 3^2)^{1/2} = \underline{\underline{4 \text{ MVAR}}}$$

$$S = VI \Rightarrow 5 \times 10^6 = 75 \times 10^3 I$$

$$\underline{\underline{I = 66\frac{2}{3} \text{ A}}}$$

Load current also flows through transmission line and voltage supply

$$ii) P_{line} = I^2 R_{line} = (66^{2/3})^2 \times 48 = \underline{213.3 \text{ kW}}$$

$$Q_{line} = I^2 X_{line} = (66^{2/3})^2 \times 240 = \underline{1.067 \text{ MVAR}}$$

By conservation of P and Q

$$\text{Real power supplied by } V_s = P_s = 213.3 \text{ kW} + 3 \text{ MW} = \underline{3.213 \text{ MW}}$$

$$Q_s = 1.067 \text{ MVAR} + 4 \text{ MVAR} = \underline{5.067 \text{ MVAR}}$$

$$\text{From the power triangle, } S_s = (P_s^2 + Q_s^2)^{1/2} = \underline{6.00 \text{ MVA}}$$

$$S_s = V_s I \Rightarrow 6 \times 10^6 = V_s \times 66^{2/3}$$

$$\underline{V_s = 90 \text{ kV}}$$

The capacitor will only affect the overall reactive power consumed i.e. The real power will remain the same. From the power triangle, for a new p.f. of 0.9:-

$$\tan \phi = \frac{Q}{P} \Rightarrow Q = P \tan \phi$$

$$\therefore \text{New } Q = 3 \times 10^6 \times \tan(\cos^{-1} 0.9) = 1.453 \text{ MVAR}$$

$$\text{New } Q = Q_{load} + Q_{capacitor} \therefore 1.453 = 4 + Q_{capacitor}$$

$$\Rightarrow Q_{capacitor} = -2.547 \text{ MVAR} = -\frac{V^2}{X_c} = -\omega C V^2$$

$$\therefore 2\pi \times 50 \times C \times (15 \times 10^3)^2 = 2.547 \times 10^6 \Rightarrow \underline{C = 1.44 \mu\text{F}}$$

$$\text{New load apparent power } S = \frac{P}{\cos \phi} = \frac{3}{0.9} = \underline{3.33 \text{ MVA}}$$

⑦

$$\therefore \text{New line current given by } S = VI \Rightarrow 3.333 \times 10^6 = 75 \times 10^3 \times I$$

$$I = 44.4 \text{ A}$$

$$\text{New line losses} = I^2 R_{\text{line}} = 44.4^2 \times 48 = 94.81 \text{ kW}$$

$$\text{Reduction in line losses} = 213.3 - 94.81 = 118.5 \text{ kW}$$

$$\% \text{ reduction} = \frac{118.5}{213.3} \times 100\% = \underline{\underline{55.6\%}}$$

$$6/1) \quad n_1 : n_2 = E_1 : E_2 = V_1 : V_2 \text{ for ideal transformer.}$$

$$= 240 : 10 = \underline{\underline{24 : 1}}$$

$$\text{ii) } \frac{V_2}{V_1} = \frac{n_2}{n_1} = \frac{1}{24} \quad \therefore V_2 = \frac{1}{24} \times V_1 = \frac{1}{24} \times 240 = \underline{\underline{10 \text{ V}}}$$

$$\text{iii) Load current} = \frac{\tilde{V}_2}{Z_2} = \frac{10}{10 + j5} = \frac{10}{(10^2 + 5^2)^{1/2}} \angle \tan^{-1} 5/10 = \frac{10}{11.2} \angle -26.6^\circ$$

$$\underline{\underline{\tilde{I}_2 = 0.894 \angle -26.6^\circ \text{ A}}}$$

$$\text{iv) } n_1 \tilde{I}_1 = n_2 \tilde{I}_2 \text{ for ideal transformer} \Rightarrow \tilde{I}_1 = \frac{n_2}{n_1} \tilde{I}_2 = \frac{1}{24} \times 0.894 \angle -26.6^\circ$$

$$\underline{\underline{\tilde{I}_1 = 0.0373 \angle -26.6^\circ \text{ A}}}$$

$$P_{\text{load}} = I_2^2 R_L = 0.894^2 \times 10 = \underline{\underline{8 \text{ W}}}$$

$$Q_{\text{load}} = I_2^2 X_L = 0.894^2 \times 5 = \underline{\underline{4 \text{ VAR}}}$$

(8)

$$P_{\text{source}} = V_1 I_1 \cos \phi = 240 \times 0.0373 \cos(26.6^\circ) = \underline{8W}$$

$$Q_{\text{source}} = V_1 I_1 \sin \phi = 240 \times 0.0373 \sin(26.6^\circ) = \underline{4VAR}$$

i.e. Ideal transformer consumes neither real or reactive power.

$$7 \text{ i)} \quad Z_L = (10 + j5) \Omega$$

$$Z_L' = \left(\frac{n_1}{n_2}\right)^2 Z_L = \left(\frac{24}{1}\right)^2 (10 + j5) = \underline{(5760 + j2880) \Omega}$$

$$\tilde{I}_1 = \frac{\tilde{V}_1}{Z_L'} = \frac{240}{5760 + j2880} = \frac{240}{6440 \angle 26.6^\circ} = \underline{0.0373 \angle -26.6^\circ A}$$

$$\text{ii)} \quad P_{\text{source}} = V_1 I_1 \cos \phi = \underline{8W} \quad Q_{\text{source}} = V_1 I_1 \sin \phi = \underline{4VAR}$$

$$8/ \text{ From o.c. test, since } \tilde{V}_1 = \tilde{E}_1 = 1000V, \tilde{V}_2 = \tilde{E}_2 = 240V$$

$$n_1 : n_2 = E_1 : E_2 = V_1 : V_2 = 1000 : 240 = \underline{4.167}$$

$$P_{oc} = \frac{V_1^2}{R_0} \Rightarrow 435 = \frac{1000^2}{R_0} \Rightarrow \underline{R_0 = 2299 \Omega}$$

$$Q_{oc} = \frac{V_1^2}{X_0} \quad \text{From power triangle, } Q_{oc} = (S_{oc}^2 - P_{oc}^2)^{1/2} \text{ where } S_{oc} = V_1 I_1$$

$$\therefore Q_{oc} = ((1000 \times 0.732)^2 - 435^2)^{1/2} = 588.7 = \frac{1000^2}{X_0}$$

$$\underline{X_0 = 1699 \Omega}$$



(9)


$$P = I_1^2 R_{t1} \Rightarrow 1089 = 16.1^2 \times R_{t1} \Rightarrow \underline{R_{t1} = 4.2 \Omega}$$

$$Q = I_1^2 X_{t1} \quad \text{Find } Q \text{ using power triangle}$$

$$S = VI_1 = 90 \times 16.1 = 1449 \text{ VA}$$

$$Q = (S^2 - P^2)^{1/2} = (1449^2 - 1089^2)^{1/2} = 955.9 \text{ VAR}$$
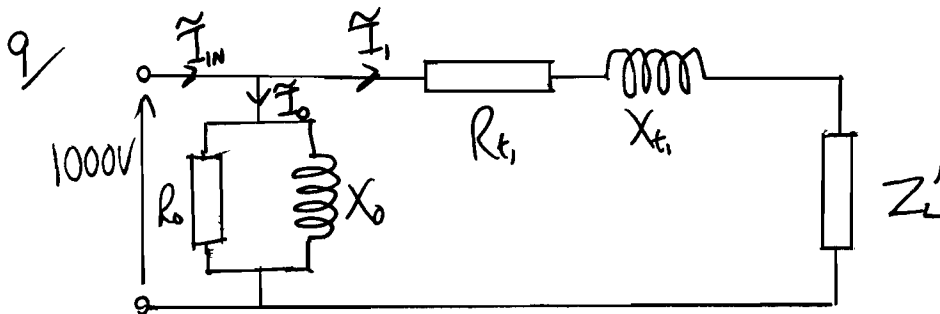
$$\therefore 955.9 = 16.1^2 \times X_{t1} \Rightarrow \underline{X_{t1} = 3.69 \Omega}$$



$$i) \quad Z_L = 3.5 + j2.7 \quad Z_L' = \left(\frac{n_1}{n_2}\right)^2 Z_L = \left(\frac{1000}{240}\right)^2 (3.5 + j2.7) = (60.76 + j46.88) \Omega$$

$$\begin{aligned} \tilde{I}_1 &= \frac{V_1}{Z_{\text{TOTAL}}} = \frac{V_1}{R_{t1} + jX_{t1} + Z_L'} = \frac{1000}{4.2 + j3.69 + 60.76 + j46.88} \\ &= \frac{1000}{64.96 + j50.57} = \frac{1000}{82.32 \angle 37.9^\circ} = \underline{12.15 \angle -37.9^\circ \text{ A}} \end{aligned}$$

$$\therefore \text{Load power} = I_1^2 R_L' = 12.15^2 \times 60.76 = \underline{8970 \text{ W}}$$

$$\text{Load reactive power} = I_1^2 X_L' = 12.15^2 \times 46.88 = \underline{6921 \text{ VAR}}$$

$$\begin{aligned} ii) \quad \text{Total input power} &= \frac{V^2}{R_0} + I_1^2 R_{t1} + P_{\text{Load}} \\ &= \frac{1000^2}{2299} + 12.15^2 \times 4.2 + 8970 = \underline{10025 \text{ W}} \end{aligned}$$

(10)

$$\begin{aligned}\text{Total input reactive power} &= \frac{V^2}{X_0} + I_1^2 X_{E1} + Q_{\text{load}} \\ &= \frac{1000^2}{1699} + 12.15^2 \times 3.69 + 6921 = \underline{\underline{8054 \text{ VAR}}}\end{aligned}$$

iii) From power triangle, input apparent power  $S_{IN} = (P_{IN}^2 + Q_{IN}^2)^{1/2}$

$$= (10025^2 + 8054^2)^{1/2} = 12859 \text{ VA} = V I_{IN} = 1000 I_{IN}$$

$$\therefore \underline{\underline{I_{IN} = 12.86 \text{ A.}}}$$

$$\cos \phi_{IN} = \frac{P_{IN}}{S_{IN}} = \frac{10025}{12859} = \underline{\underline{0.780 \text{ lagging.}}}$$

$$\rho = \frac{P_{\text{LOAD}}}{P_{IN}} = \frac{8970}{10025} = 0.895 \text{ i.e. } \underline{\underline{89.5\%}}$$

$$\text{Load apparent power } S_L = (P_L^2 + Q_L^2)^{1/2} = (8970^2 + 6921^2)^{1/2} = 11330 \text{ VA}$$

$$S_L = V_L I_L = V_L' I_L' = V_L' I_1 \Rightarrow 11330 = V_L' \times 12.15$$

$$V_L' = 932.5 \text{ V}$$

$$\therefore \frac{V_L}{V_L'} = \frac{n_2}{n_1} = \frac{240}{1000} \Rightarrow V_L = \frac{24}{100} \times 932.5 \text{ V} = \underline{\underline{223.8 \text{ V}}}$$

$$\text{Regulation} = \frac{V_{2oc} - V_2}{V_{2oc}} = \frac{240 - 223.8}{240} \times 100\% = \underline{\underline{6.75\%}}$$